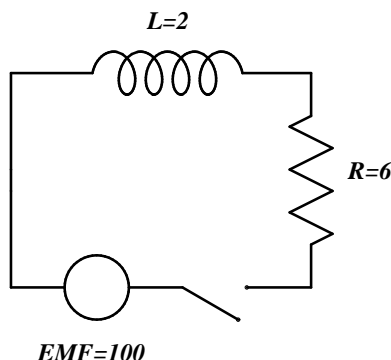


**II. Example 2: R-L DC Circuit**

Physical characteristics of the circuit: 100 volt DC battery connected in series with a 2 henry inductor and a 6 ohm resistor; current flows when the open switch is closed.

**Questions:**

- [a] Describe in words how the current changes over time.
- [b] What is the current 1 second after the switch is closed?
- [c] At what time does the current equal 8 amps?
- [d] At what time does the current equal  $k$  amps, where  $k$  is a positive constant?

**Solution of Circuit IVP:**

By Kirchhoff's laws we have  $E_L + E_R = EMF$  which, with  $E_L = L \cdot I'(t)$  and  $E_R = R \cdot I(t)$ , translates into the following Initial Value Problem (for  $t \geq 0$ ):

$$2I'(t) + 6I(t) = 100, \quad I(t) = 0 \quad \text{at} \quad t = 0$$

We can solve for  $I$  using a method called *separation of variables*. First, we will divide through by 2, replace  $I(t)$  by  $I$ , and use the differential notation for derivatives:

$$\frac{dI}{dt} + 3I = 50$$

Solving for  $\frac{dI}{dt}$  shows that this is not a simple integration problem because the derivative of  $I$  depends on both  $t$  and  $I$

$$\frac{dI}{dt} = 50 - 3I \tag{*}$$

**Outline of solution** by *separation of variables*

Use algebra to rewrite (\*) as

$$\frac{dI}{50 - 3I} = dt$$

and integrate both sides to obtain

$$-\frac{1}{3} \ln |50 - 3I| = t + C$$

which with the initial condition  $I(0) = 0$  yields the circuit current


$$I(t) = \frac{50}{3} (1 - e^{-3t}), \quad t \geq 0$$

More details for all these steps may be found below, after the Answers.
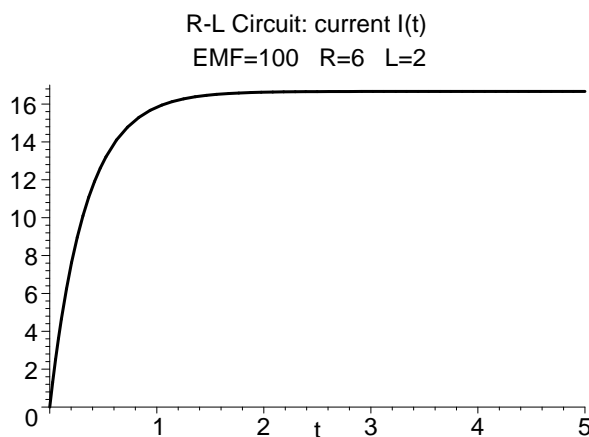
### Answers:

[a] Describe in words how the current changes over time.


The following graph shows how  $I(t)$  increases from 0 at  $t = 0$  toward an asymptotic limit  $50/3$  as  $t$  increases. This asymptotic limit is called the *steady-state* current.



[b] What is the current 1 second after the switch is closed?

$$I(1) = \frac{50}{3} (1 - e^{-3}) \approx 15.84$$

which agrees with the following graph.

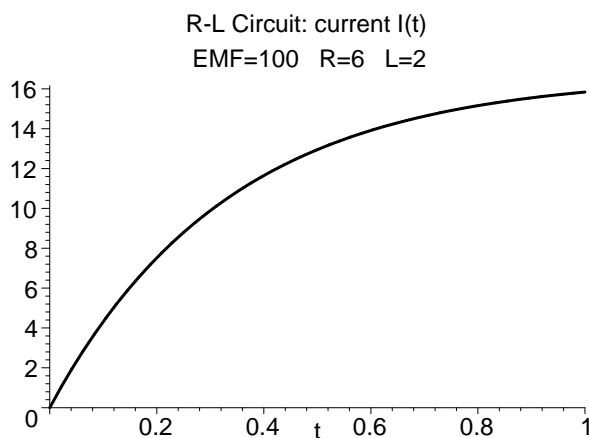

[c] At what time does the current equal 8 amps?

Solve

$$\frac{50}{3} (1 - e^{-3 \cdot t}) = 8$$

to get  $t = -\frac{1}{3} \ln \left( \frac{13}{25} \right) \approx 0.22$ , which agrees with the preceding graph.

[d] At what time does the current equal  $k$  amps, where  $k$  is a positive constant?

Using the same steps as in the preceding part

$$t = -\frac{1}{3} \ln \left( 1 - \frac{3k}{50} \right)$$

for any  $k < 50/3$ .

**Details of solution** by *separation of variables*

After multiplying both sides of the ODE

$$\frac{dI}{dt} = 50 - 3I \quad (*)$$

by  $dt$ , we get the ODE in differential form

$$dI = (50 - 3I) dt$$

Divide both sides by  $50 - 3I$  in order to *separate variables: put anything involving  $I$  on one side and anything involving  $t$  on the other side*:

$$\frac{dI}{50 - 3I} = dt \quad (1)$$

Now we are allowed to integrate each side separately and still have equality. The right side of equation (1) is easy:

$$\int dt = t + C$$

where  $C$  is an arbitrary constant. The left side of equation (1) looks related to the integral  $\int \frac{1}{x} dx$ . So we use the substitution

$$\begin{aligned} x &= 50 - 3I \\ \text{to get } \frac{dx}{dI} &= -3 \\ \text{or } dI &= -\frac{1}{3} dx \end{aligned}$$

Then in equation (1) we replace  $50 - 3I$  with  $x$  and  $dI$  with  $-\frac{1}{3}dx$  and integrate in order to get the left side to equal

$$\begin{aligned} \int \frac{1}{50 - 3I} dI &= \int \frac{1}{x} \left( -\frac{1}{3} dx \right) \\ &= -\frac{1}{3} \int \frac{1}{x} dx \\ &= -\frac{1}{3} \ln |x| + C \\ &= -\frac{1}{3} \ln |50 - 3I| + C \end{aligned}$$

Hence equation (1), after both sides are integrated, becomes (collecting all arbitrary constants on the right hand side as a single arbitrary constant)

$$-\frac{1}{3} \ln |50 - 3I| = t + C \quad (2)$$

Since there is no current when the switch is thrown, we let  $I = 0$  when  $t = 0$  to solve for  $C$

$$-\frac{1}{3} \ln |50 - 0| = 0 + C \implies C = -\frac{1}{3} \ln 50$$

and so equation (2) becomes

$$-\frac{1}{3} \ln |50 - 3I| = -\frac{1}{3} \ln 50 + t$$

It is usually preferable to solve for the dependent variable,  $I$  in this case. To do that, we first multiply both sides of the last equation by  $-3$  to get

$$\ln |50 - 3I| = \ln 50 - 3t$$

then take the exponential (inverse logarithm) of both sides

$$e^{\ln |50 - 3I|} = e^{\ln 50 - 3t} \tag{3}$$

and then use a property of exponentials

$$e^{a+b} = e^a \times e^b$$

with  $a = \ln 50$  and  $b = -3t$  to get from equation (3)

$$\begin{aligned} |50 - 3I| &= e^{\ln 50} \times e^{-3t} \\ &= 50e^{-3t} \end{aligned}$$

since  $e^{\ln 50} = 50$ . Now  $|x| = c \implies x = \pm c$  so we have

$$50 - 3I = \pm 50e^{-3t}$$

Since we know that  $I = 0$  at  $t = 0$ , we determine the sign to be  $+$ , allowing us to solve for  $I$  by dividing both sides of the last equation by 3 and then isolating  $I$  on one side

$$I(t) = \frac{50}{3} (1 - e^{-3t}), \quad t \geq 0$$